

Sequential Circuit

State Machines and Registers

Ver. 3

Professor: Yang Peng




Topics

- Characteristic and Excitation Tables
- Designing circuits to function as Finite State Machines
 - Example 1: Two-bit binary counter
 - Example 2: Three-bit sequential circuit
- Looking at Typical Sequential Circuits
 - Ripple counter
 - Shift register
 - Storage register

Null Ch3.7

Burger Ch5

Characteristic Table for FF

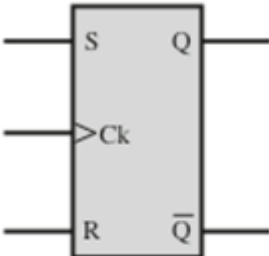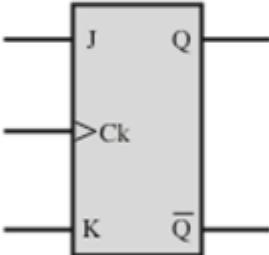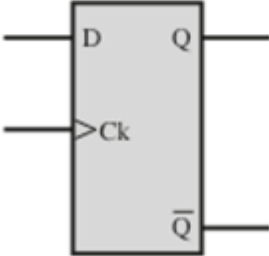Name	Graphical Symbol	Characteristic Table															
S-R		<table><tr><th>S</th><th>R</th><th>Q_{n+1}</th></tr><tr><td>0</td><td>0</td><td>Q_n</td></tr><tr><td>0</td><td>1</td><td>0</td></tr><tr><td>1</td><td>0</td><td>1</td></tr><tr><td>1</td><td>1</td><td>—</td></tr></table>	S	R	Q_{n+1}	0	0	Q_n	0	1	0	1	0	1	1	1	—
S	R	Q_{n+1}															
0	0	Q_n															
0	1	0															
1	0	1															
1	1	—															
J-K		<table><tr><th>J</th><th>K</th><th>Q_{n+1}</th></tr><tr><td>0</td><td>0</td><td>Q_n</td></tr><tr><td>0</td><td>1</td><td>0</td></tr><tr><td>1</td><td>0</td><td>1</td></tr><tr><td>1</td><td>1</td><td>$\overline{Q_n}$</td></tr></table>	J	K	Q_{n+1}	0	0	Q_n	0	1	0	1	0	1	1	1	$\overline{Q_n}$
J	K	Q_{n+1}															
0	0	Q_n															
0	1	0															
1	0	1															
1	1	$\overline{Q_n}$															
D		<table><tr><th>D</th><th>Q_{n+1}</th></tr><tr><td>0</td><td>0</td></tr><tr><td>1</td><td>1</td></tr></table>	D	Q_{n+1}	0	0	1	1									
D	Q_{n+1}																
0	0																
1	1																

State, Characteristic, and Excitation Tables




- **State Transition Table:** Give the next state information based on the input and current state (like truth table)
- **Characteristic Table:** Give the state transition information based on inputs (simplified state transition table)
- **Excitation Table** (inverted characteristic table)
 - **Input:** current state and next state
 - **Output:** S R or J K or D – the control bit(s) of FF
 - Necessity
 - To understand how to set the control bits to generate a needed state transition
 - If you know the excitation table, you know how the sequential circuit can be built

Excitation Table for Flip-Flops

SR flip-flop				D flip-flop		
$Q(t)$	$Q(t + 1)$	S	R	$Q(t)$	$Q(t + 1)$	D
0	0	0	×	0	0	0
0	1	1	0	0	1	1
1	0	0	1	1	0	0
1	1	×	0	1	1	1

JK flip-flop			
$Q(t)$	$Q(t + 1)$	J	K
0	0	0	×
0	1	1	×
1	0	×	1
1	1	×	0

“X” is the “don’t care” state

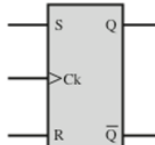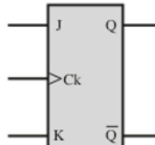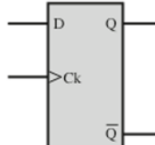
Name	Graphical Symbol	Characteristic Table															
S-R		<table><tr><th>S</th><th>R</th><th>Q_{n+1}</th></tr><tr><td>0</td><td>0</td><td>Q_n</td></tr><tr><td>0</td><td>1</td><td>0</td></tr><tr><td>1</td><td>0</td><td>1</td></tr><tr><td>1</td><td>1</td><td>—</td></tr></table>	S	R	Q_{n+1}	0	0	Q_n	0	1	0	1	0	1	1	1	—
S	R	Q_{n+1}															
0	0	Q_n															
0	1	0															
1	0	1															
1	1	—															
J-K		<table><tr><th>J</th><th>K</th><th>Q_{n+1}</th></tr><tr><td>0</td><td>0</td><td>Q_n</td></tr><tr><td>0</td><td>1</td><td>0</td></tr><tr><td>1</td><td>0</td><td>1</td></tr><tr><td>1</td><td>1</td><td>$\overline{Q_n}$</td></tr></table>	J	K	Q_{n+1}	0	0	Q_n	0	1	0	1	0	1	1	1	$\overline{Q_n}$
J	K	Q_{n+1}															
0	0	Q_n															
0	1	0															
1	0	1															
1	1	$\overline{Q_n}$															
D		<table><tr><th>D</th><th>Q_{n+1}</th></tr><tr><td>0</td><td>0</td></tr><tr><td>1</td><td>1</td></tr></table>	D	Q_{n+1}	0	0	1	1									
D	Q_{n+1}																
0	0																
1	1																

Design of Finite State Machines


- 5 Steps
 1. Draw a state transition diagram
 2. Draw a state transition table
 3. *Simplify redundant states (not always necessary)*
 4. Allocate flip-flop output signals to the states
 5. Draw K-maps to design combinational logics that generates state transitions and outputs

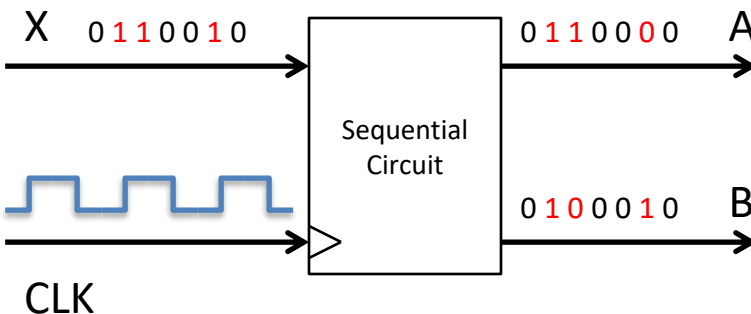Example 1: 2-Bit Binary Counter

- The input is a binary stream
- Count the number of encountered 1s in the input signal, from 0 to 3, (i.e., 00 to 11) and thereafter reset to 0, (i.e., 00)



Step 1: State Diagram

 

Step 2: State Transition Table

	Input X = 0			Input X = 1		
Current State	Next State	Output A	Output B	Next State	Output A	Output B
S0	S0	0	0	S1	0	1
S1	S1	0	1	S2	1	0
S2	S2	1	0	S3	1	1
S3	S3	1	1	S0	0	0

Step 3: Simplification Skipped

No States to Merge in this example

Step 4: State Allocation

State allocation to two JK FFs: A and B

State	AB
S0	00
S1	01
S2	10
S3	11

JK FF's Excitation Table

Qt	Qt+1	J	K
0	0	0	*
0	1	1	*
1	0	*	1
1	1	*	0


State Transition Table with JK FFs: A and B

	Input X = 0		Input X = 1		Input X=0		Input X=1		Input X=0		Input X=1	
Current State	Next State	Output	Next State	Output	Inputs to JK FF-A				Inputs to JK FF-B			
A _t B _t	A _{t+1} B _{t+1}	A _{t+1} B _{t+1}	A _t B _t	A _{t+1} B _{t+1}	JA	KA	JA	KA	JB	KB	JB	KB
00	00	00	01	01	0	*	0	*	0	*	1	*
01	01	01	10	10	0	*	1	*	*	0	*	1
10	10	10	11	11	*	0	*	0	0	*	1	*
11	11	11	00	00	*	0	*	1	*	0	*	1

Step 5: Karnaugh Maps

State Transition Table with JK FF A and B

	Input X = 0		Input X = 1		Input X=0		Input X=1		Input X=0		Input X=1	
Current State	Next State	Output	Next State	Output	Inputs to JK FF-A				Inputs to JK FF-B			
A _t B _t	A _{t+1} B _{t+1}	A _{t+1} B _{t+1}	A _t B _t	A _{t+1} B _{t+1}	JA	KA	JA	KA	JB	KB	JB	KB
00	00	00	01	01	0	*	0	*	0	*	1	*
01	01	01	10	10	0	*	1	*	*	0	*	1
10	10	10	11	11	*	0	*	0	0	*	1	*
11	11	11	00	00	*	0	*	1	*	0	*	1

 

$J_A = BX$

	AB	00	01	11	10
X					
0		0	0	*	*
1		0	1	*	*

$J_B = X$

	AB	00	01	11	10
X					
0		0	*	*	0
1		1	*	*	1


$K_A = BX$

	AB	00	01	11	10
X					
0		*	*	0	0
1		*	*	1	0

$K_B = X$

	AB	00	01	11	10
X					
0		*	0	0	*
1		*	1	1	*



Logic of 2-bit Binary Counter

 


Example 2: 3-bit Sequential Circuit

- An input is a sequence of 3-bit binary numbers.
- If it is sequence 111, 110, 011, or 010, the circuit should emit 1 as its output; otherwise, the circuit emits 0.

Step 1: State Diagram

  

Step 2: State Transition Diagram

 

	Input X = 0		Input X = 1	
Current State	Next State	Output Z	Next State	Output Z
S0	S2	0	S1	0
S1	S4	0	S3	0
S2	S6	0	S5	0
S3	S0	1	S0	1
S4	S0	0	S0	0
S5	S0	1	S0	1
S6	S0	0	S0	0

Step 3: Simplification

	Input X = 0		Input X = 1	
Current State	Next State	Output Z	Next State	Output Z
S0	S2	0	S1	0
S1	S46	0	S35	0
S2	S46	0	S35	0
S35	S0	1	S0	1
S46	S0	0	S0	0

Coldwell's merging rule:

States that transit to the same state and produces the same output can be merged

Step 3: Simplification

	Input X = 0		Input X = 1	
Current State	Next State	Output Z	Next State	Output Z
S0	S12	0	S12	0
S12	S46	0	S35	0
S35	S0	1	S0	1
S46	S0	0	S0	0

Four states left after merging: S0, S12 (new S1), S35 (new S2), S46 (new S3)

Step 4: State Allocation

State allocation to two JK FFs: A and B

State	AB
S0	00
S1 (S12)	01
S2 (S35)	11
S3 (S46)	10

JK FF's Excitation Table

Qt	Qt+1	J	K
0	0	0	*
0	1	1	*
1	0	*	1
1	1	*	0

State Transition Table with JK FFs: A and B

	Input X = 0		Input X = 1		Input X=0		Input X=1		Input X=0		Input X=1	
Current State	Next State	Output	Next State	Output	Inputs to JK FF-A				Inputs to JK FF-B			
A _t B _t	A _{t+1} B _{t+1}	Z	A _{t+1} B _{t+1}	Z	JA	KA	JA	KA	JB	KB	JB	KB
00	01	0	01	0	0	*	0	*	1	*	1	*
01	10	0	11	0	1	*	1	*	*	1	*	0
11	00	1	00	1	*	1	*	1	*	1	*	1
10	00	0	00	0	*	1	*	1	0	*	0	*

Step 5: Karnaugh Maps

State Transition Table with JK FFs: A and B

	Input X = 0		Input X = 1		Input X=0		Input X=1		Input X=0		Input X=1	
Current State	Next State	Output	Next State	Output	Inputs to JK FF-A				Inputs to JK FF-B			
A _t B _t	A _{t+1} B _{t+1}	Z	A _{t+1} B _{t+1}	Z	JA	KA	JA	KA	JB	KB	JB	KB
00	01	0	01	0	0	*	0	*	1	*	1	*
01	10	0	11	0	1	*	1	*	*	1	*	0
11	00	1	00	1	*	1	*	1	*	1	*	1
10	00	0	00	0	*	1	*	1	0	*	0	*

$J_A = B$


$J_B = \sim A$

$K_A = 1$

$K_B = \sim X + A$

$$Z = AB\sim X + ABX = AB(\sim X + X) = AB$$

3-bit Sequential Circuit's Circuit

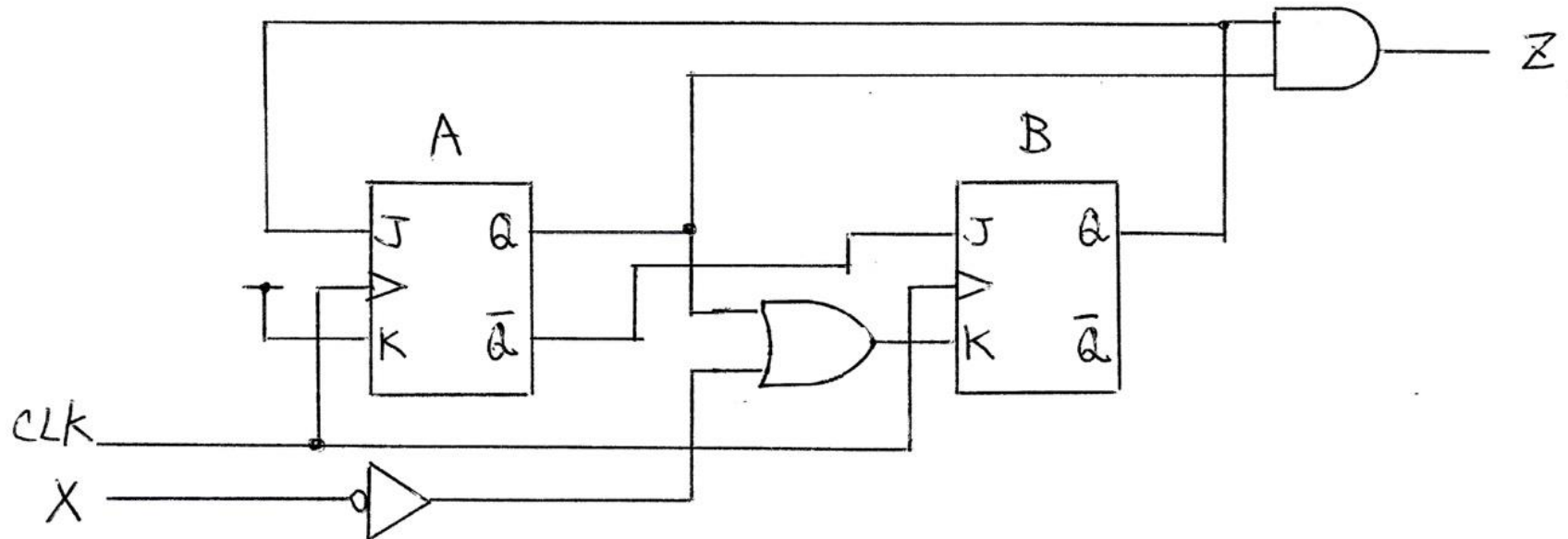

How about Allocating D FF?

State allocation to two D FFs: A and B

State	AB
S0	00
S1 (S12)	01
S2 (S35)	11
S3 (S46)	10

D FF State Transition Table

Qt	Qt+1	D
0	0	0
0	1	1
1	0	0
1	1	1

State Transition Table with D FFs: A and B

	Input X = 0		Input X = 1		Input X = 0	Input X = 1	Input X = 0	Input X = 1
Current State	Next State	Output	Next State	Output	Inputs to D FF-A		Inputs to D FF-B	
$A_t B_t$	$A_{t+1} B_{t+1}$	Z	$A_{t+1} B_{t+1}$	Z	D_A	D_A	D_B	D_B
00	01	0	01	0	0	0	1	1
01	10	0	11	0	1	1	0	1
11	00	1	00	1	0	0	0	0
10	00	0	00	0	0	0	0	0

Kmap and D FF-based Circuit

State Transition Table with D FFs: A and B

	Input X = 0		Input X = 1		Input X = 0	Input X = 1	Input X = 0	Input X = 1
Current State	Next State	Output	Next State	Output	Inputs to D FF-A		Inputs to D FF-B	
$A_t B_t$	$A_{t+1} B_{t+1}$	Z	$A_{t+1} B_{t+1}$	Z	D_A	D_A	D_B	D_B
00	01	0	01	0	0	0	1	1
01	10	0	11	0	1	1	0	1
11	00	1	00	1	0	0	0	0
10	00	0	00	0	0	0	0	0

$$D_A = \sim AB$$

AB \ Y	00	01	11	10
0	0	1	0	0
1	0	1	0	0


Kmap

$$D_B = \tilde{A}\tilde{B} + \tilde{A}X$$

$$= \tilde{A}(\tilde{B} + X)$$



AB \ X	00	01	11	10
0	1	0	0	0
1	1	1	0	0

Kmap

 


$$Z = AB(\sim X + X) = AB$$

  D FF connected in a divide-by-two configuration




D Flip-Flops as a Ripple Counter

 - A 4-bit binary *ripple counter*
 - Given the name because the pulses “ripple” through the circuit




- Each “D” FF divides the incoming clock frequency by 2X
- RESET sets all Q output to 0 without a clock signal (asynchronous)
- Counts as fast as the first stage can toggle, but cannot be read until the count has rippled through to the last stage
- Can build counter/dividers of any length, any binary divisor
 - Clock frequency at output Q_3 equals $f_{\text{Clock in}} \div 16$

D Flip-Flops as a Shift Register

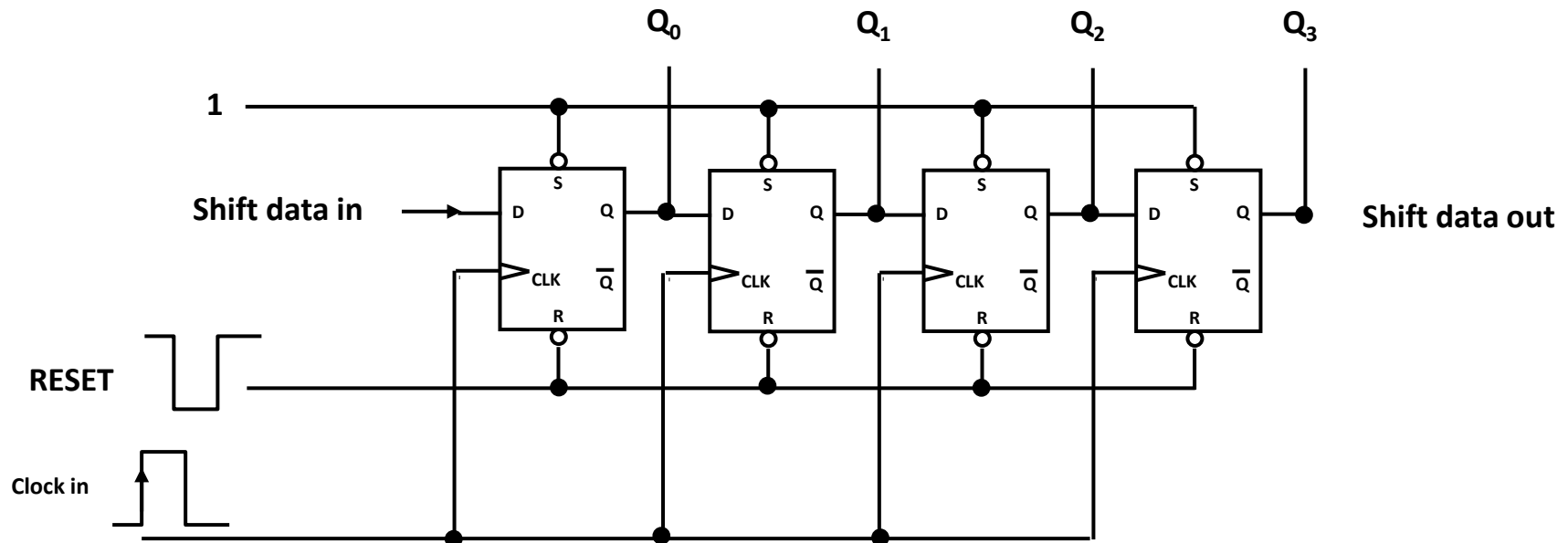


- Shift register moves data through successive stages on each clock pulse
- Used for serial data communications, multiplication, image processing
- Basis for UART (*Universal Asynchronous Receiver/Transmitter*)
- Data can be read in serially and then read out in parallel
- Serial data communications limits the number of signal wires needed to transmit byte-wide data

D Flip-Flops as a Storage Register

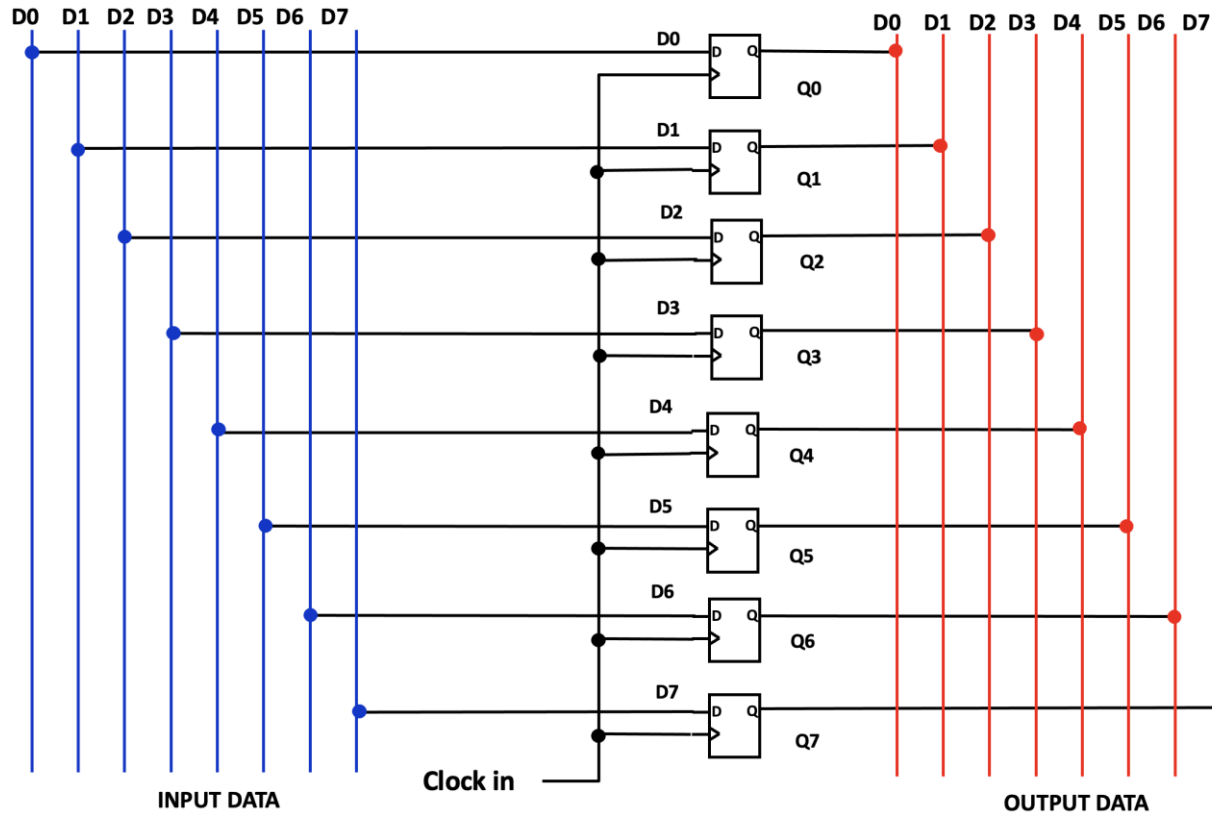

 - **BUS:** A grouping of “like” signals
Here we have Data In bus (D0..D7) and Data out bus (Q0..Q7)
- **Busses are usually drawn with** heavier lines to differentiate them from individual signal wires



Summary

- Understand how to design and implement a finite state machine with flip-flops.
- Review typical sequential circuits that are used in computer design.