

Sequential Circuit

Flip Flops / Memory Components

Ver. 3

Professor: Yang Peng

Topics

- 1-Bit Memory Devices
 - Latches (event-driven devices)
 - SR Latch
 - JK Latch
 - D Latch
 - Flip-Flops (clock-driven devices)
 - JK Flip-Flop
 - D Flip-Flop


Burger Ch 4 and 5.

Null Ch 3.

Combinational vs. Sequential Circuit


Combinational

- No state and time

 

Sequential

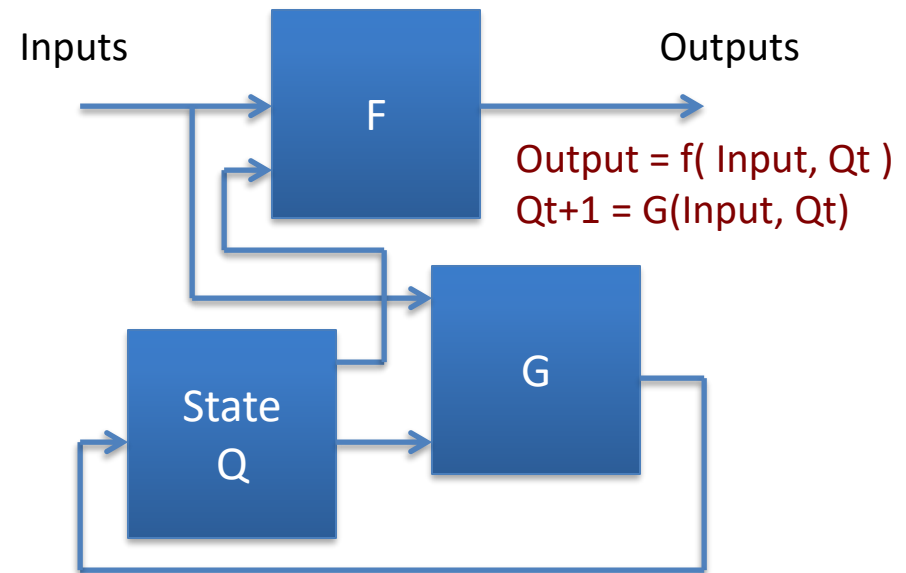- Maintaining states
- States transiting along time with inputs and the current states



Asynchronous vs. Synchronous Logic

Event-driven (Asynchronous)


- States and outputs change with random events.
- 1-bit memory device: Latch
 - SR Latch
 - D Latch

Clock-driven (Synchronous)

- States and outputs change with periodic clock signals.
- 1-bit memory device: Flip-Flop
 - D Flip-Flop
 - JK Flip-Flop



Characteristic Table

S	R	Q_{n+1}
0	0	Q_n
0	1	0
1	0	1
1	1	—

 

A	B	NOR
0	0	1
0	1	0
1	0	0
1	1	0


SR Latch

  

When $S=1$ and $R=1$, the output will be in “race condition” (forbidden state)

SR Latch

Active Low


 


active
low




\bar{S}	\bar{R}	Q	\bar{Q}	
<u>L</u>	H	H	L	Set
H	<u>L</u>	L	H	Reset
H	H	Q_{n-1}	\bar{Q}_{n-1}	No change (latch)
L	L	H	H	Undefined

Active High
(Textbook Spec.)

S	R	Q_{n+1}
0	0	Q_n
0	1	0
1	0	1
1	1	—

  

SR Latch Application: Switch Debouncer

   


Clocks and Time

- The **clock** in a digital system is an electronic analog of the pendulum which synchronizes the circuits in a computer system
 - The master control signal
 - Changes occur on the rising or falling edges of a clock pulse
- Frequencies are the inverse of time (speed)


Frequency		Speed	Time
1 kilohertz	KHz	10^3 Hz	1msec
1 megahertz	MHz	10^6 Hz	1μsec
IBM PC (with Intel 486)	50 MHz		20nsec
1 gigahertz	GHz	10^9 Hz	1nsec
Dell Precision T550 (Intel Xeon X5698)	4.4 GHz		
1 terahertz	THz	10^{12} Hz	1psec

This is the TTL (74 series) level.

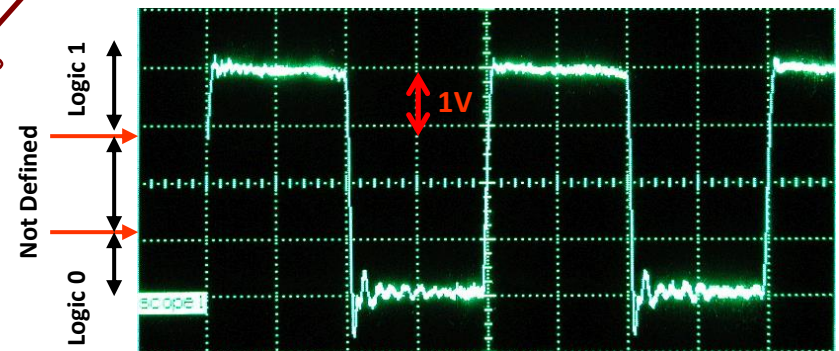


Clocks and Pulses

 - Clocks are continuous streams of pulses



 
- Duty cycle = $t_{PH} / (t_{PH} + t_{PL}) \times 100\%$
 - The clock signal shown above has a 50% duty cycle
 - The clock signal shown below has a 25% duty cycle
 - **Period:** The time to complete one clock cycle
 - Period = t_{cycle}
 - **Frequency:** The inverse of the period, $f = 1/\text{period}$



Clocked SR Latch and D Latch


Clocked SR Latch

 - Prevent the latch from changing state except at certain specific time.
- When clock is 1, the latch is sensitive to S or R.




Clocked D Latch

 - **Avoid the SR latch's instability by giving R as the inverse of S.**
- Stored value is available at Q
- To load the current value of D, give a positive pulse on the clock line.



Clocked JK Latch

 
- Avoid the SR latch's instability by preventing the inputs being 1 at the same time.
- In this case all possible combinations of input values are valid!



C	J	K	Q	\bar{Q}
0	0	0	latch	latch
0	0	1	0	1
0	1	0	1	0
0	1	1	toggle	toggle
x	0	0	latch	latch
x	0	1	latch	latch
x	1	0	latch	latch
x	1	1	latch	latch


Issue with Clock Signal

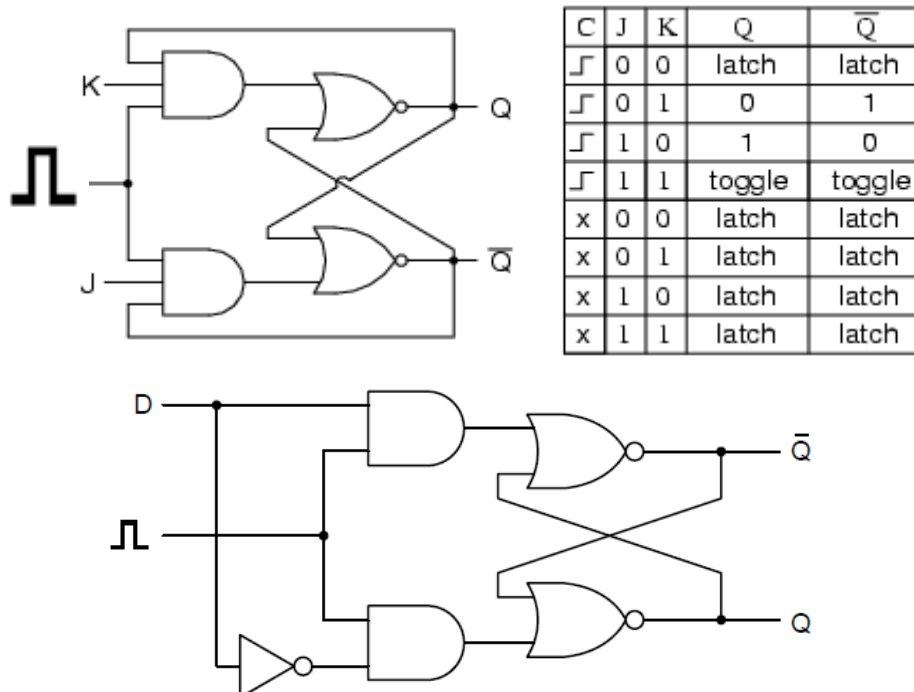- What if the input signal (J and K in JK Latch or D in D latch) gets changed when the clock is HIGH?





Creating an Edge




 
- Delay in the inverter makes the circuit work!







$\Delta t = 12.60\text{ns}$

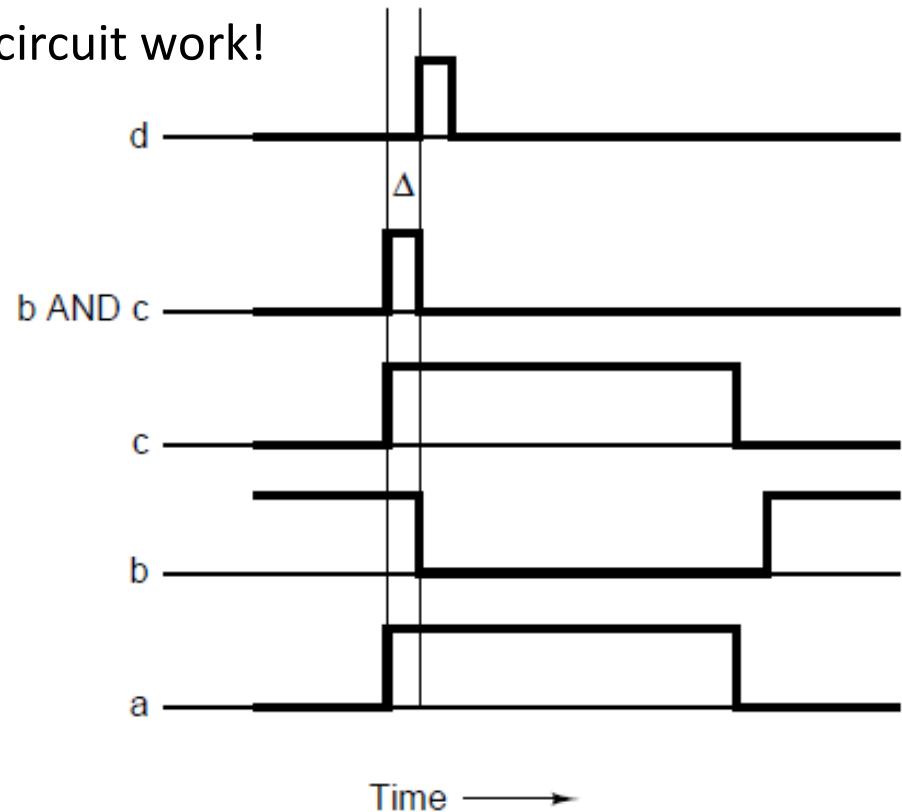 


Rising-Edge Pulse Detector

    


Falling-Edge Pulse Detector

    

Using Pulse Detector in Circuit

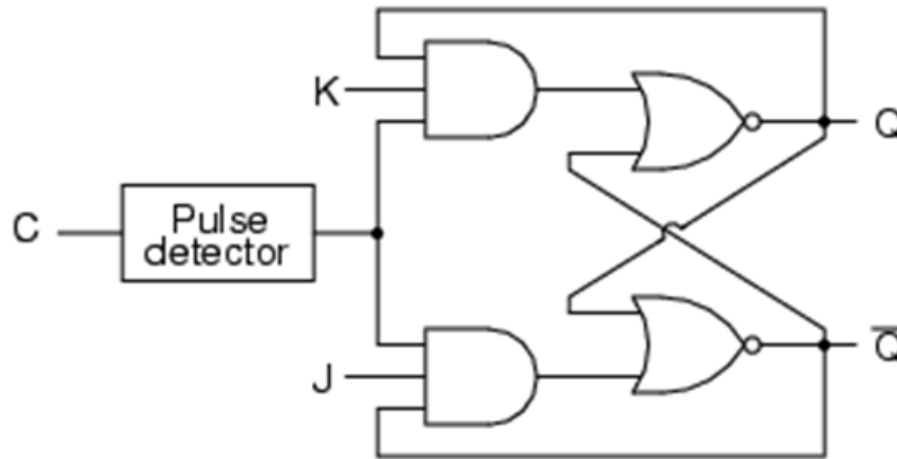

Now called JK Flip-Flop

 


Now called D Flip-Flop

Latch vs. Flip-Flop

	Latch	Flip-Flop
Similarities	<ul style="list-style-type: none">• Basic components for sequential circuit design• They are bi-state devices. It is in one of two states.• Without inputs, they remain in that state.• They have two outputs which are always the complements of each other.	
Differences	Level triggered: State changes when the clock is active.	Edge triggered: State transition occurs when the clock transition from 0 to 1 or from 1 to 0.

D Flip-Flop and JK Flip-Flop

 

D	clk	Q	\bar{Q}
L	↑	L	H
H	↑	H	L
*	L	Q_0	\bar{Q}_0


Set upon an up edge of the clock

D	clk	Q State	J	K	JK/FF CLK
0	↑	0 Reset	0	1	↓
1	↑	1 Set	1	0	↓
*	0	Q_0 No Change	*	*	1

$$J = D$$


$$K = \bar{D}$$
 
$$\text{JK/FF's CLK} = \overline{D/\text{FF's CLK}}$$




D Flip-Flop Application

D-FF

 




Application 1: Data Register

D-FF

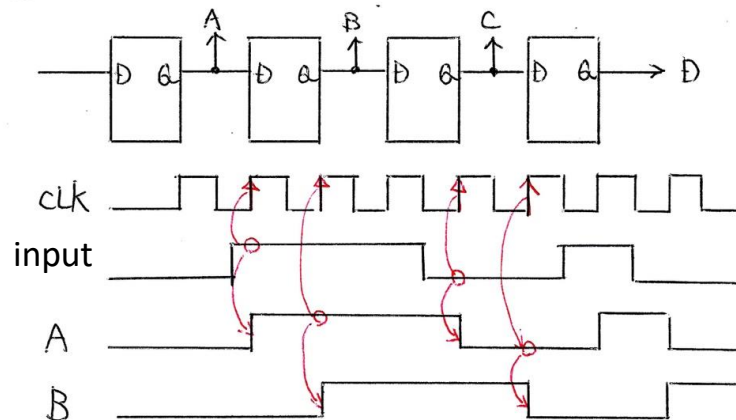

Application 2: Shift Register

Characteristic Table for FF

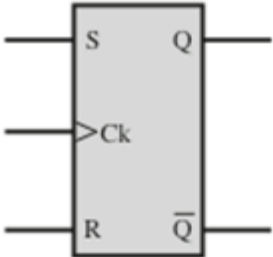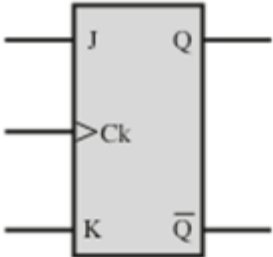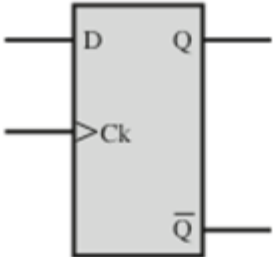Name	Graphical Symbol	Characteristic Table															
S-R		<table><tr><th>S</th><th>R</th><th>Q_{n+1}</th></tr><tr><td>0</td><td>0</td><td>Q_n</td></tr><tr><td>0</td><td>1</td><td>0</td></tr><tr><td>1</td><td>0</td><td>1</td></tr><tr><td>1</td><td>1</td><td>—</td></tr></table>	S	R	Q_{n+1}	0	0	Q_n	0	1	0	1	0	1	1	1	—
S	R	Q_{n+1}															
0	0	Q_n															
0	1	0															
1	0	1															
1	1	—															
J-K		<table><tr><th>J</th><th>K</th><th>Q_{n+1}</th></tr><tr><td>0</td><td>0</td><td>Q_n</td></tr><tr><td>0</td><td>1</td><td>0</td></tr><tr><td>1</td><td>0</td><td>1</td></tr><tr><td>1</td><td>1</td><td>$\overline{Q_n}$</td></tr></table>	J	K	Q_{n+1}	0	0	Q_n	0	1	0	1	0	1	1	1	$\overline{Q_n}$
J	K	Q_{n+1}															
0	0	Q_n															
0	1	0															
1	0	1															
1	1	$\overline{Q_n}$															
D		<table><tr><th>D</th><th>Q_{n+1}</th></tr><tr><td>0</td><td>0</td></tr><tr><td>1</td><td>1</td></tr></table>	D	Q_{n+1}	0	0	1	1									
D	Q_{n+1}																
0	0																
1	1																

Summary

- Understand the difference between latches and flip-flops
- Understand the reason why
 - Transiting from SR to JK latches
 - Transiting from JK latch to master-slave JK flip-flop
- Understand what applications use SR latch and D flip-flop