 


# Autumn 2022, Homework 5 Key

**Q1. (2 pts)** Consider the logic gate circuit shown below.



**Q1-1.** To derive a Boolean equation for x. You don't need to simplify the Boolean equation in this step.

$$x = \sim(\sim(a \text{ XOR } c) + \sim b) * (\sim(\sim b(b + d)))$$

**Grading: the result should be the same as this provided answer.**

**If the result does not match, -0.5.**

**Q1-2.** Simplify the equation, using the Boolean algebra for output x. The result must be shown in the most simplified format.

$$\begin{aligned} x &= ((a \text{ XOR } c) * b) * (b + \sim(b + d)) \quad // \text{ de Mogen's law} \\ &= a \text{ XOR } c * b * b + a \text{ XOR } c * b * (\sim b * \sim d) \quad // b * \sim b \text{ must be } 0 \\ &= a \text{ XOR } c * b \end{aligned}$$

**Grading: the result should be the same as this provided answer. Or, the XOR part could be extended, i.e., the final result is:  $x = (a \sim c + \sim a c) * b = ab \sim c + \sim a bc$**

**If the result does not match, -0.5.**

**If the progress is not shown, even when the result is correct, -0.5.**

**Q2. (9pts)** Design a combinational circuit system.

Design a combinational circuit with three inputs x, y, z, and three outputs A, B, C. Note that both xyz and ABC represent a three-bit binary number where x and A are the most significant bits, whereas z and C are the least significant bits. When a binary input xyz is 4 (100), 5 (101), 6 (110), or 7 (111), the binary output ABC is two less than the input xyz. When the binary input is 0 (000), 1 (001), 2 (010), or 3 (011), the binary output ABC is two more than the input xyz.

Please answer all of the following sub-questions.

**Q2-1. (1pt)** Draw a truth table of inputs xyz and outputs ABC.

Inputs			Outputs		
x	y	z	A	B	C
0	0	0	0	1	0
0	0	1	0	1	1
0	1	0	1	0	0
0	1	1	1	0	1
1	0	0	0	1	0
1	0	1	0	1	1
1	1	0	1	0	0
1	1	1	1	0	1

**Grading: any mistake, -0.5.**

**Q2-2. (3pts)** Based on the truth table you draw, build a Karnaugh map for each output of A, B, and C. In other words, you have to draw A's K-map, B's K-map, and C's K-map respectively.

A's K-map

xy \ z	00	01	11	10
0	0	1	1	0
1	0	1	1	0

B's K-map

xy \ z	00	01	11	10
0	1	0	0	1
1	1	0	0	1

C's K-map

xy \ z	00	01	11	10
0	0	0	0	0
1	1	1	1	1

**Grading: for each table, any mistake, -0.5.**

**Q2-3. (3pts)** Derive (as simple as possible) Boolean equations for A, B, and C using the Karnaugh maps.

$$A = y$$

$$B = \sim y$$

$$C = z$$

**Grading: for each equation, any mistake, -0.5.**

**Q2-4. (1pt)** Based on the Boolean equations, draw the logical gate diagram (circuit) for this system in Logisim. **Copy and paste the circuit (or capture the diagram) in this submission. (No .circ file is necessary.)**

**Grading: If the circuit is not attached, -1.  
The correctness of the circuit is evaluated by the next question.**

**Q2-5. (1pt)** Test your circuit with the Logisim simulation and generate the truth table (In Logisim, project-->analyze circuit-->table). **Copy and paste the table (or capture the table) in this submission.**

**Grading: If the table is manually drawn, -1.**

**Q3. (9pts) Design a 2-bit by 2-bit multiplier.**

In the class, we discussed about how to build a 2-bit by 2-bit multiplier using two half adders. (See slide deck 10. CpuComponentAluDesign.pptx). To eliminate a propagation delay with a ripple carry, design the same multiplier through KMaps, thus without cascading two half adders.

**Q3-1. (1pt)** Fill out the following truth table.

A	* B	= C	A <sub>1</sub>	A <sub>0</sub>	B <sub>1</sub>	B <sub>0</sub>	C <sub>3</sub>	C <sub>2</sub>	C <sub>1</sub>	C <sub>0</sub>
0	0	0	0	0	0	0	0	0	0	0
0	1	0	0	0	0	1	0	0	0	0
0	2	0	0	0	1	0	0	0	0	0
0	3	0	0	0	1	1	0	0	0	0
1	0	0	0	1	0	0	0	0	0	0
1	1	1	0	1	0	1	0	0	0	1
1	2	2	0	1	1	0	0	0	1	0
1	3	3	0	1	1	1	0	0	1	1
2	0	0	1	0	0	0	0	0	0	0
2	1	2	1	0	0	1	0	0	1	0
2	2	4	1	0	1	0	0	1	0	0
2	3	6	1	0	1	1	0	1	1	0
3	0	0	1	1	0	0	0	0	0	0
3	1	3	1	1	0	1	0	0	1	1
3	2	6	1	1	1	0	0	1	1	0
3	3	9	1	1	1	1	1	0	0	1

**Grading: any mistake in this table, -0.5.**

**Q3-2. (2pts)** From the truth table, derive the Boolean equations, each representing C<sub>0</sub> and C<sub>3</sub>. Their Boolean equations are too simple to use a KMap.

$$C_0 = \sim A_1 A_0 \sim B_1 B_0 + \sim A_1 A_0 B_1 B_0 + A_1 A_0 \sim B_1 B_0 + A_1 A_0 B_1 B_0, \text{ or, } C_0 = A_0 B_0$$

$$C_3 = A_1 A_0 B_1 B_0$$

**Grading: any mistake in each equation, -0.5.**

**Q3-3. (2pt)** Draw a KMap for C2. Derive the Boolean equation to represent C2.

$A_1A_0 \backslash B_1B_0$	00	01	11	10
00	0	0	0	0
01	0	0	0	0
11	0	0	0	1
10	0	0	1	1

$$C_2 = A_1 \sim A_0 B_1 + A_1 B_1 \sim B_0 = A_1 B_1 (\sim A_0 + \sim B_0)$$

Or,  $C_2 = A_1 B_1 \sim (A_0 B_0)$

**Grading: any mistake in the table, -0.5. Any mistake in the equation, -0.5.**

**Q3-4. (2pt)** Draw a KMap for C1. Derive the Boolean equation to represent C1.

$A_1A_0 \backslash B_1B_0$	00	01	11	10
00	0	0	0	0
01	0	0	1	1
11	0	1	0	1
10	0	1	1	0


$$C_1 = A_1 \sim B_1 B_0 + A_1 \sim A_0 B_0 + \sim A_1 A_0 B_1 + A_0 B_1 \sim B_0$$

$$= A_1 B_0 (\sim A_0 + \sim B_1) + A_0 B_1 (\sim A_1 + \sim B_0)$$

Or,  $C_1 = A_1 B_0 \sim (A_0 B_1) + A_0 B_1 \sim (A_1 B_0) = (A_0 B_1) \text{ XOR } (A_1 B_0)$

**Grading: any mistake in the table, -0.5. Any mistake in the equation, -0.5.**

 **Q3-5. (1pt)** Based on the Boolean equations, draw this multiplier logic in Logisim. Copy and paste the circuit (or capture the diagram) in your submission. (No .circ file is necessary.)



**Grading: If the circuit is not attached, -1.**  
**The correctness of the circuit is evaluated by the next question.**

**Q3-6. (1pt)** Test your circuit with the Logisim simulation and generate the truth table. **Copy and paste the table (or capture the table) in your submission.**

a	b	c	d	x	y	z	u
0	0	0	0	0	0	0	0
0	0	0	1	0	0	0	0
0	0	1	0	0	0	0	0
0	0	1	1	0	0	0	0
0	1	0	0	0	0	0	0
0	1	0	1	0	0	0	1
0	1	1	0	0	0	1	0
0	1	1	1	0	0	1	1
1	0	0	0	0	0	0	0
1	0	0	1	0	0	1	0
1	0	1	0	0	1	0	0
1	0	1	1	0	1	1	0
1	1	0	0	0	0	0	0
1	1	0	1	0	0	1	1
1	1	1	0	0	1	1	0
1	1	1	1	1	0	0	1

**Grading: If the table is manually drawn, -1. Any mistake in this table, -0.5.**