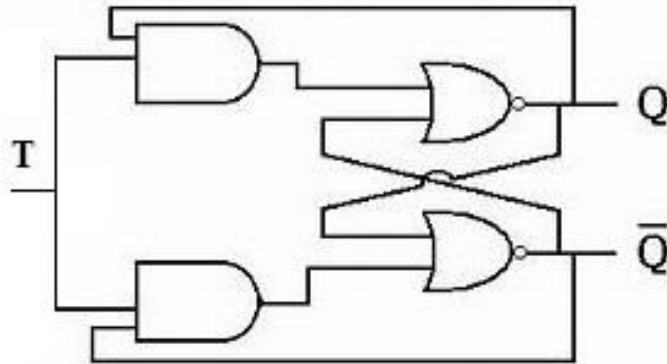


Quiz 12 – to be finished in 15 minutes

Student Name:

Question 1

The following circuit represents a T latch.



| A | B | NOR |
|---|---|-----|
| 0 | 0 | 1 |
| 0 | 1 | 0 |
| 1 | 0 | 0 |
| 1 | 1 | 0 |

Refer the above circuit and NOR gate truth table, fill out the state table for T latch.

Tip: $Q(t+1)$ could be “0”, “1”, “ $\sim Q(t)$ ” representing one time change from the previous state, “ $Q(t)$ ” representing no change from the previous state, or “Toggle” representing repeated changes between “0” and “1”. You just need to decide what $Q(t+1)$ should be.

| T | $Q(t)$ | $\sim Q(t)$ | $Q(t+1)$ | $\sim Q(t+1)$ |
|---|--------|-------------|----------------|---------------------|
| 0 | 0 | 1 | 0 (or $Q(t)$) | 1 (or $\sim Q(t)$) |
| 0 | 1 | 0 | 1 (or $Q(t)$) | 0 (or $\sim Q(t)$) |
| 1 | 0 | 1 | Toggle | Toggle |
| 1 | 1 | 0 | Toggle | Toggle |

2 pts for each row

If row 3 shows “1 0”, 1 point off

If row 4 shows “0 1”, 1 point off