

Bus and Memory Design

Ver. 2

Professor: Yang Peng

Microprocessor

This is what CPU does not include.

D0..D31

DATA

Memory

A0..A31

Data Write

Sign Extender

Data Read

Register Files
r0 – r15

Rd

Program
Counter
r15

Rn
A

Rm
B

Acc

Barrel
Shifter

ALU

Multiply
Accumulate
(MAC)

Result
Rd

ADDRESS

Address
Register


Incrementer

Instruction
Decoder


Peripherals

CPU and Memory

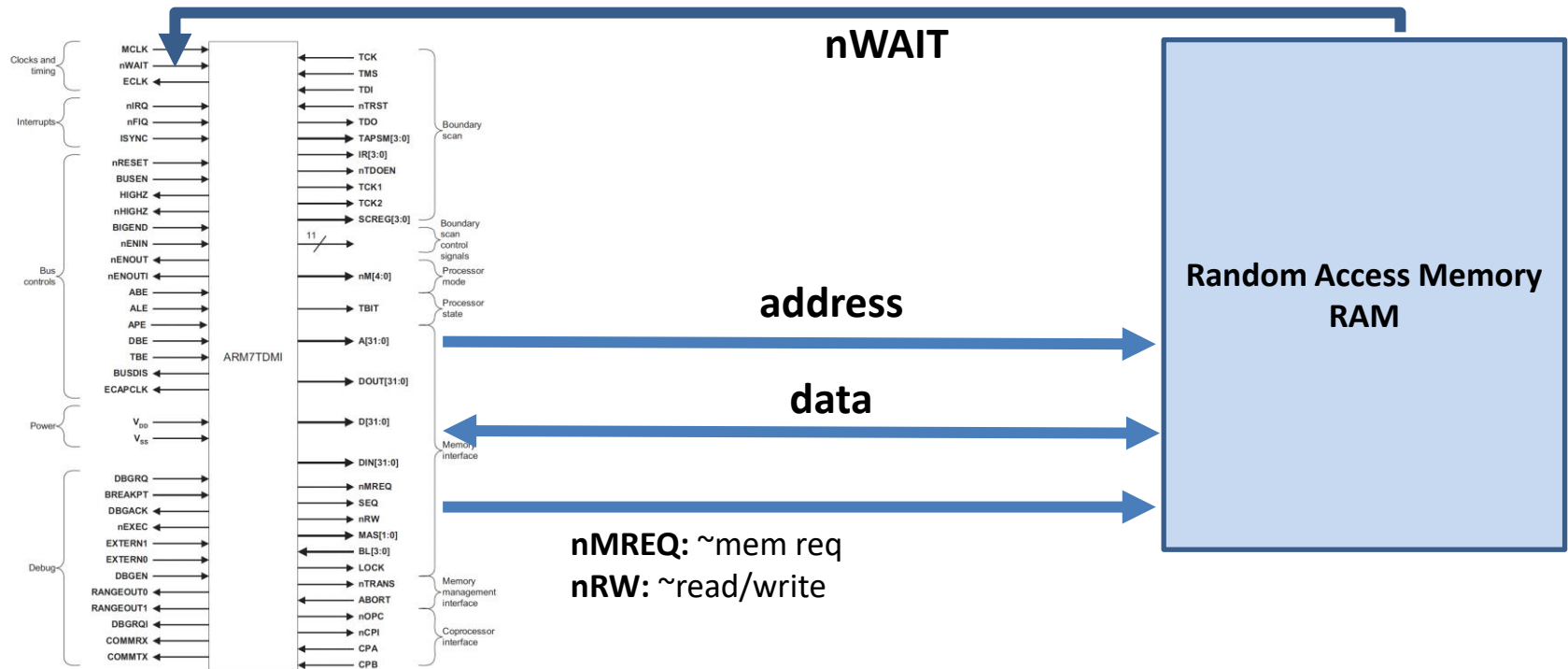- CPU has only temporary storage, the registers, for computation
- Most data should be maintained in external memory
 - ROM (Read-Only Memory): code, const data
 - RAM (Random Access Memory): can store (after loading) your programs and data
- CPU-memory communication takes place with **address**, **data**, and **control** signals.



Memory Capacity

 


Memory capacity: $2^K \times N$

- Suppose a memory chip has 16 address lines and 8 data lines

What is the capacity of the chip?

- _____ bits
 - _____ bytes (8 bits)
 - _____ words (16 bits)
-
- Suppose a chip has a capacity of $2^K \times 16$, how many address bits and data bits?
 - _____ address bits
 - _____ data bits

Memory Organization



 


4 addresses x 4 bits/address = 16 bits = 2 bytes

Memory Extension

- Large memory chip can be constructed with several smaller size of memory chips
- AS6C4008 is an SRAM with the capacity of 19×8 .
- CY7C187 is an SRAM with the capacity of 16×1 .
- How to arrange CY7C187s to replace an AS6C4008 with them?

  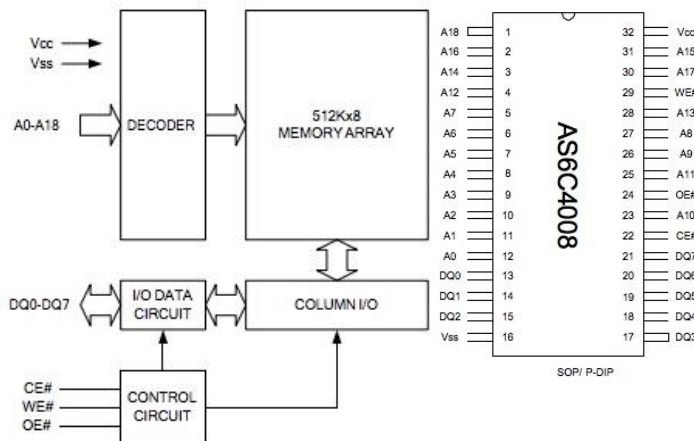
3 more address lines
= decoded to 2^3 different chip enables




In total, $(2^{19} \times 8) / (2^{16} \times 1) = 2^3 \times 8 = 64$

8 data lines

Increase Address Spaces

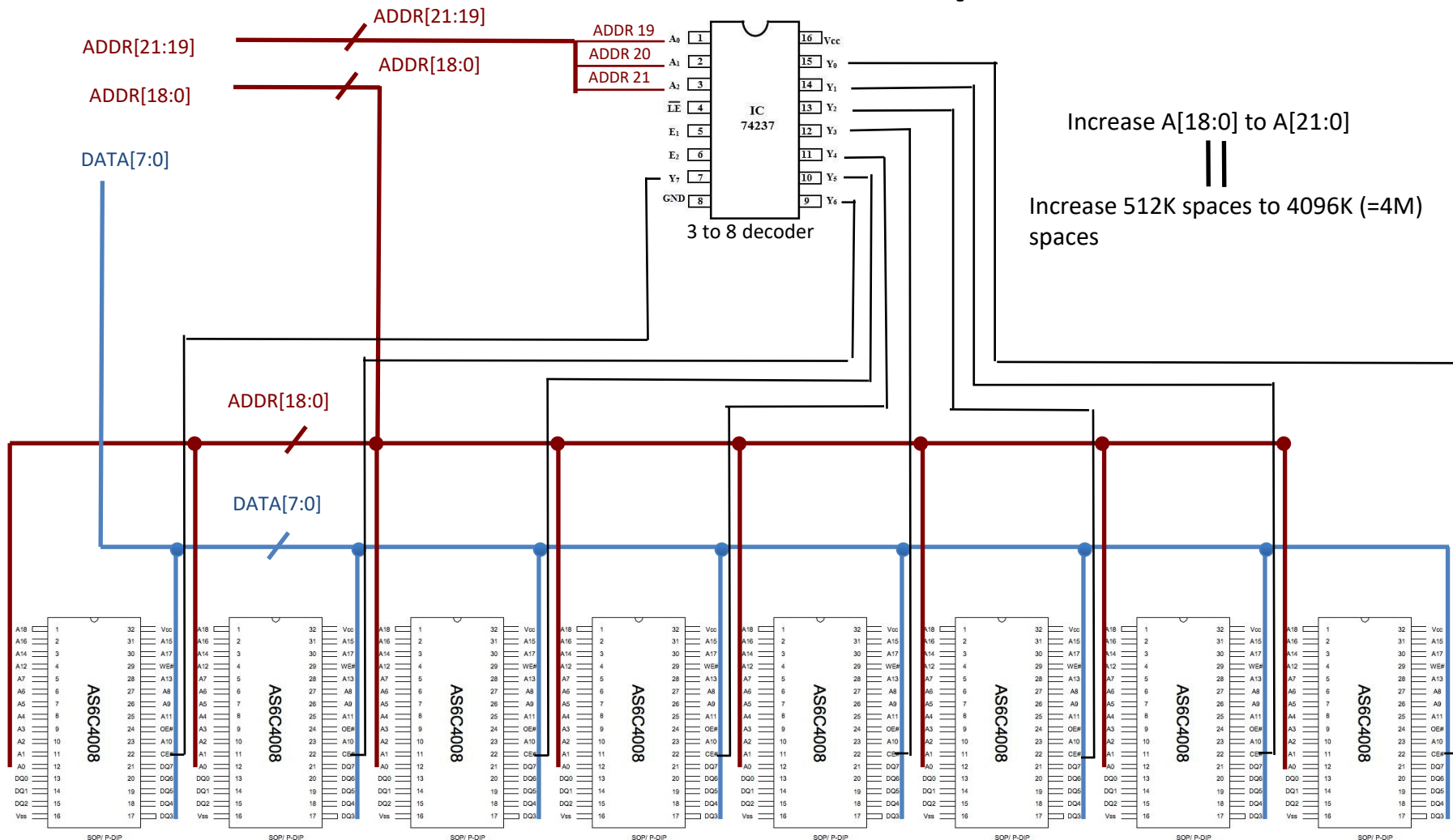

Increase Data Width

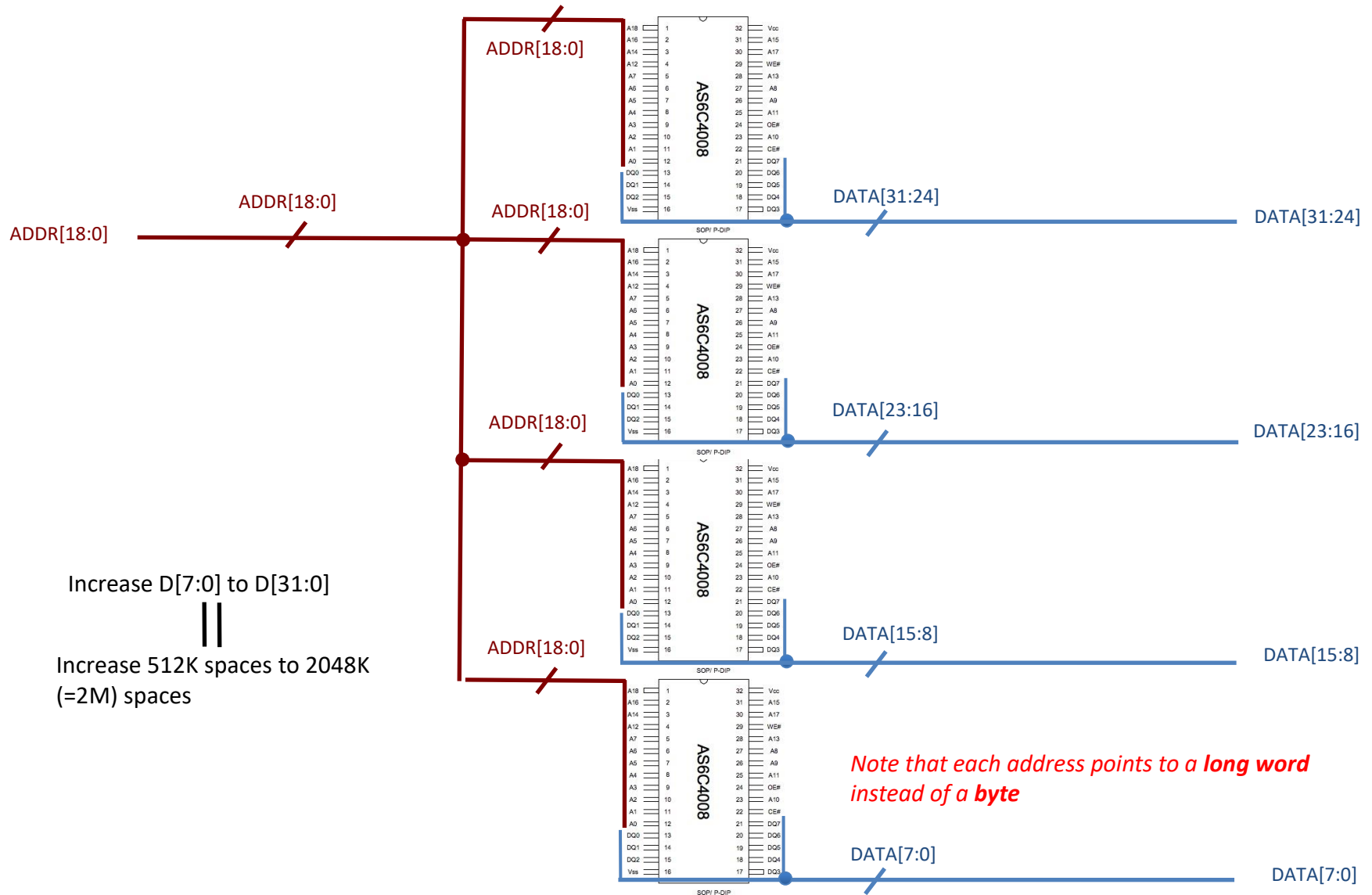

Increase Both

- Increase the address length
- Increase the data width
- Exercise:
 - Build a $2^{24} \times 32$ memory using $2^{19} \times 8$ memory chips
 - How many $2^{19} \times 8$ memory chips should you have?

$$(2^{24} \times 32) / (2^{19} \times 8) = 2^5 \times 4 = 128 \text{ chips}$$

24-19 = 5 additional address lines


- How many 3-to-8 decoders do you need to activate 128 CE lines?

four 8-bit chips (32 bits) in a row, $128/4 = 32$ rows.

Select 1 out of 32 rows, need $32/8 = 4$ 3-8 decoders

Select 1 out of 4 decoders, need 1 3-8 decoder


5 decoders in total!

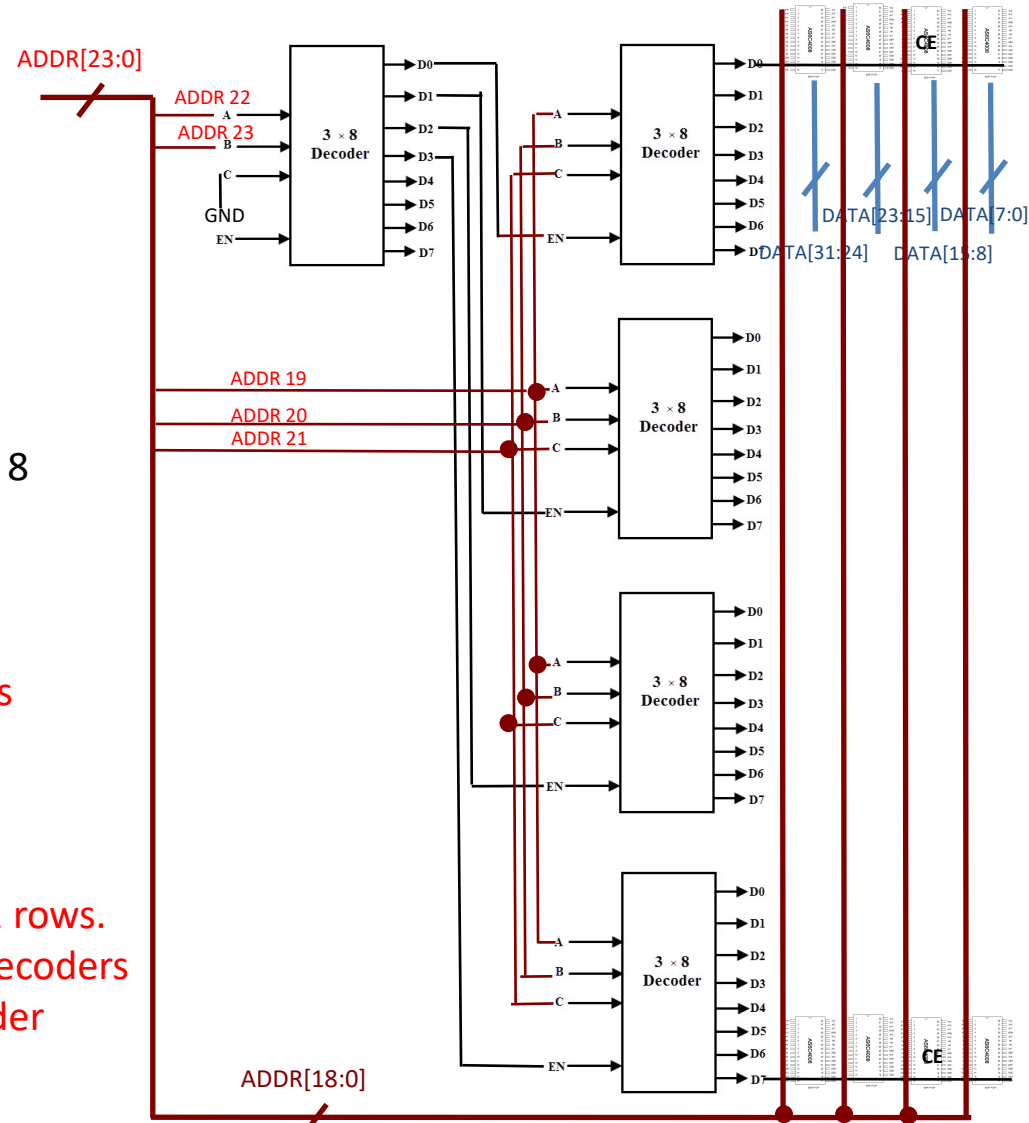

Bus and I/O


Ver. 2

Bus Organization

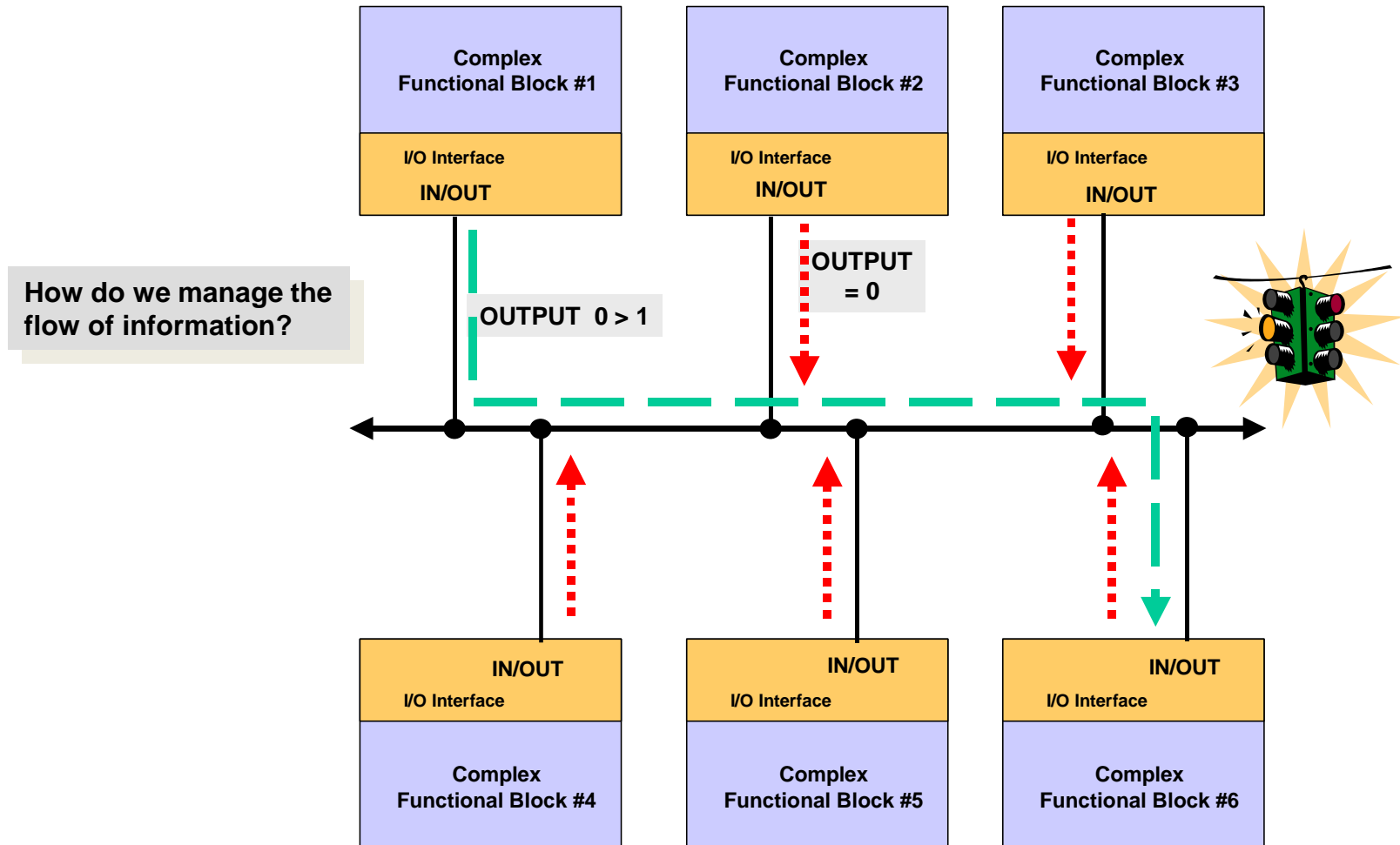

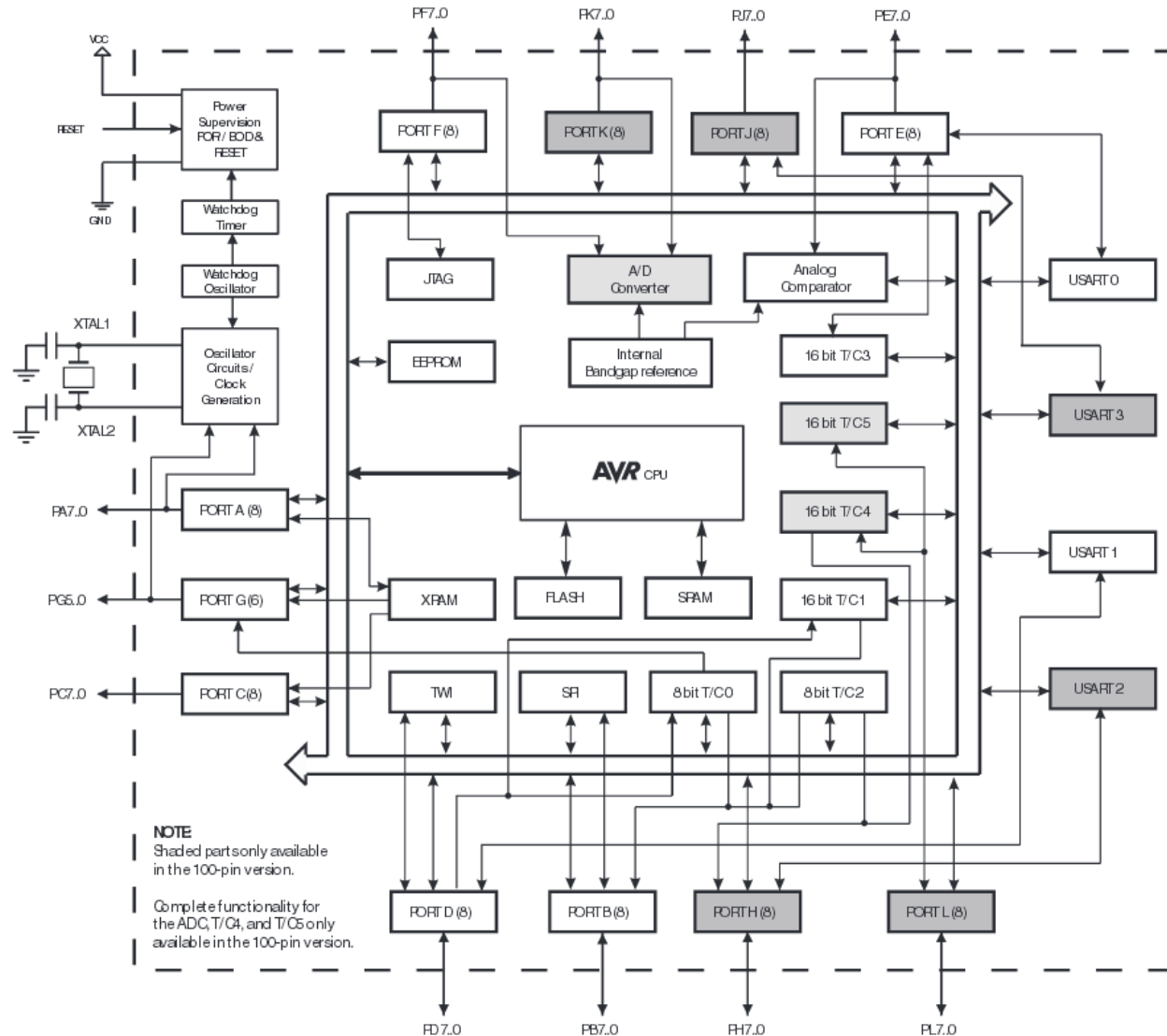
Example Bus Connection

- Busses were invented in order to simplify the organization and flow of data within computer systems
 - Busses allow many devices to connect to the same data path
 - Allow for efficient exchange of data between devices




Bus Collision

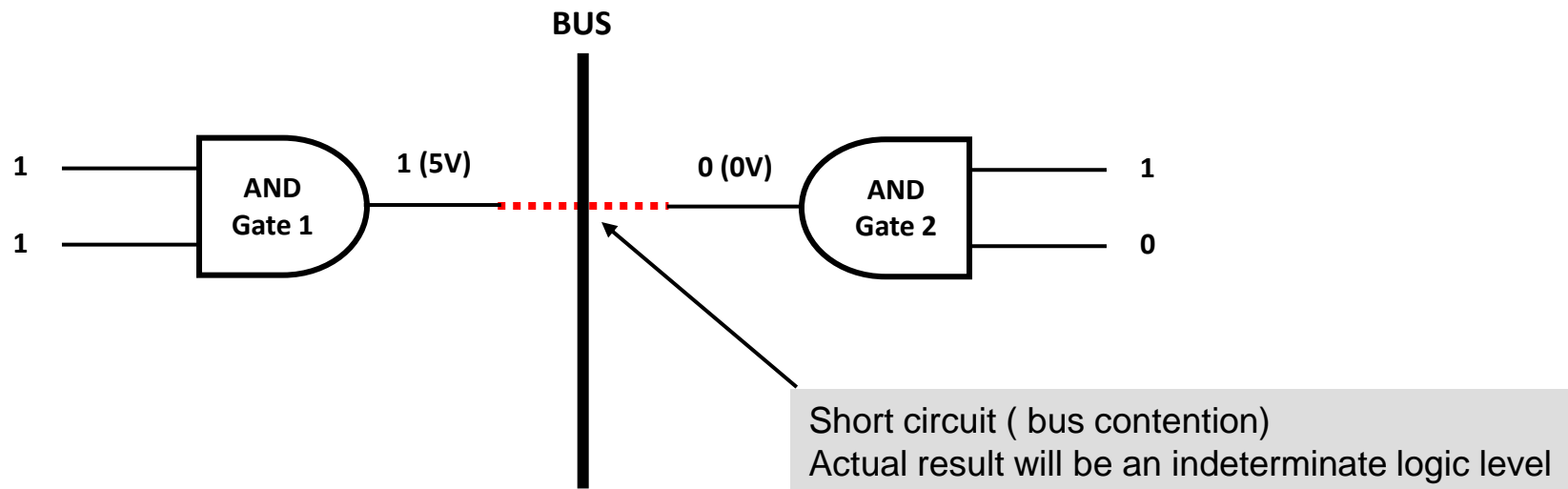- **Question:** How do I connect outputs together and not get a short circuit?



Bus Arbitration

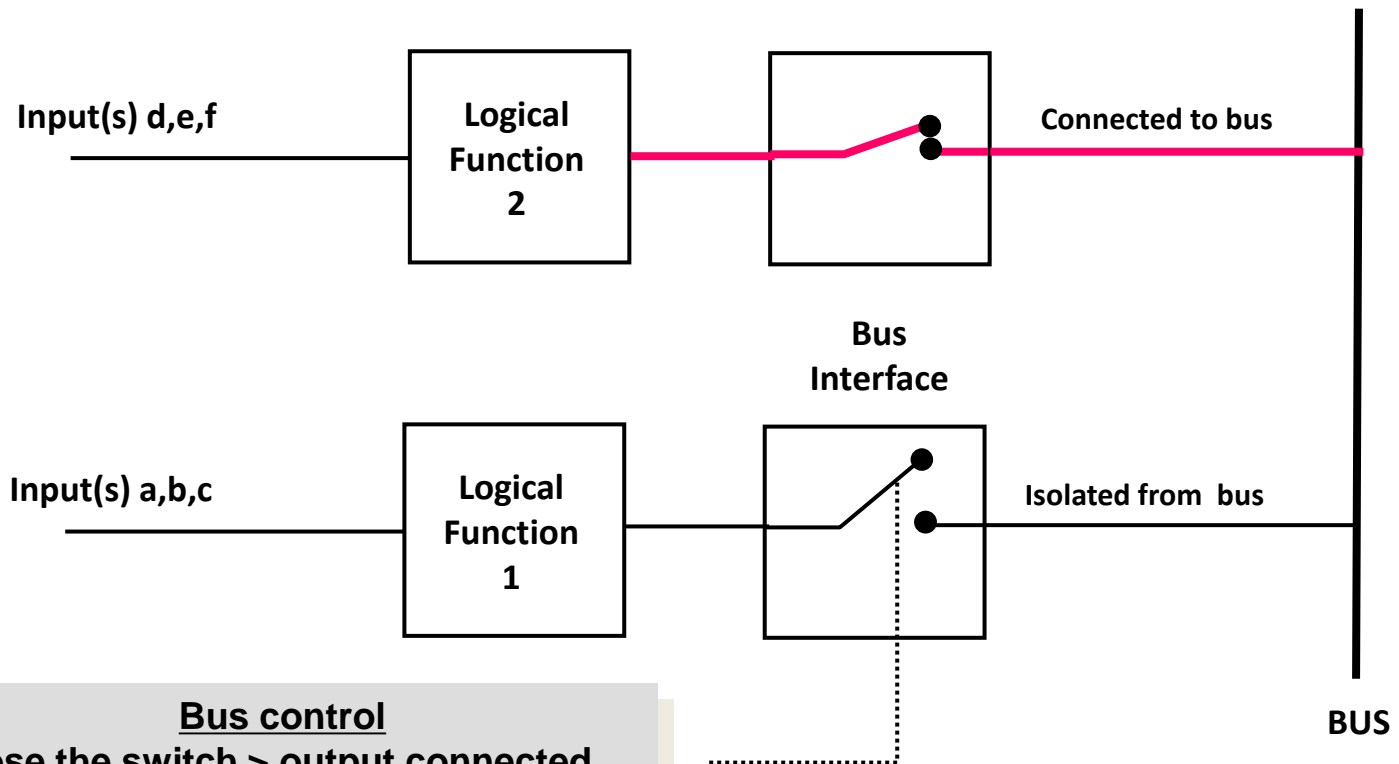

Bus control


- Close the switch > output connected
- Open the switch > output disconnected

Bus Interface Structure: Tristate

Truth table for **Bus Interface Gate**


Output Enable	INPUT	OUTPUT
0	1	1
0	0	0
1	1	Hi Z
1	0	Hi Z

Bus Interface Gate

 

Hi Z: removing the gate
from the circuit


Memory Organization

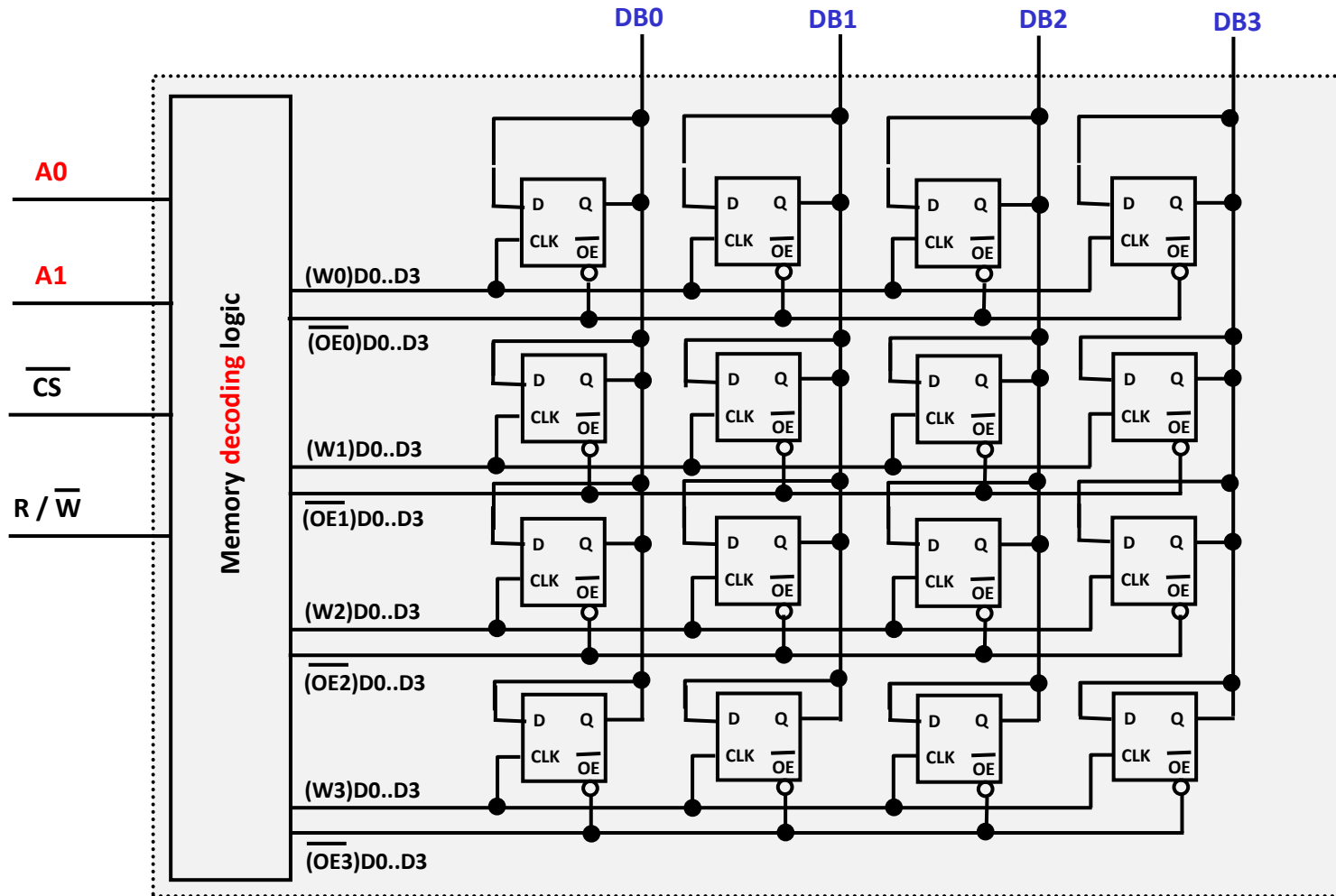

4 addresses x 4 bits/address = 16 bits = 2 bytes


Memory-Mapped I/O

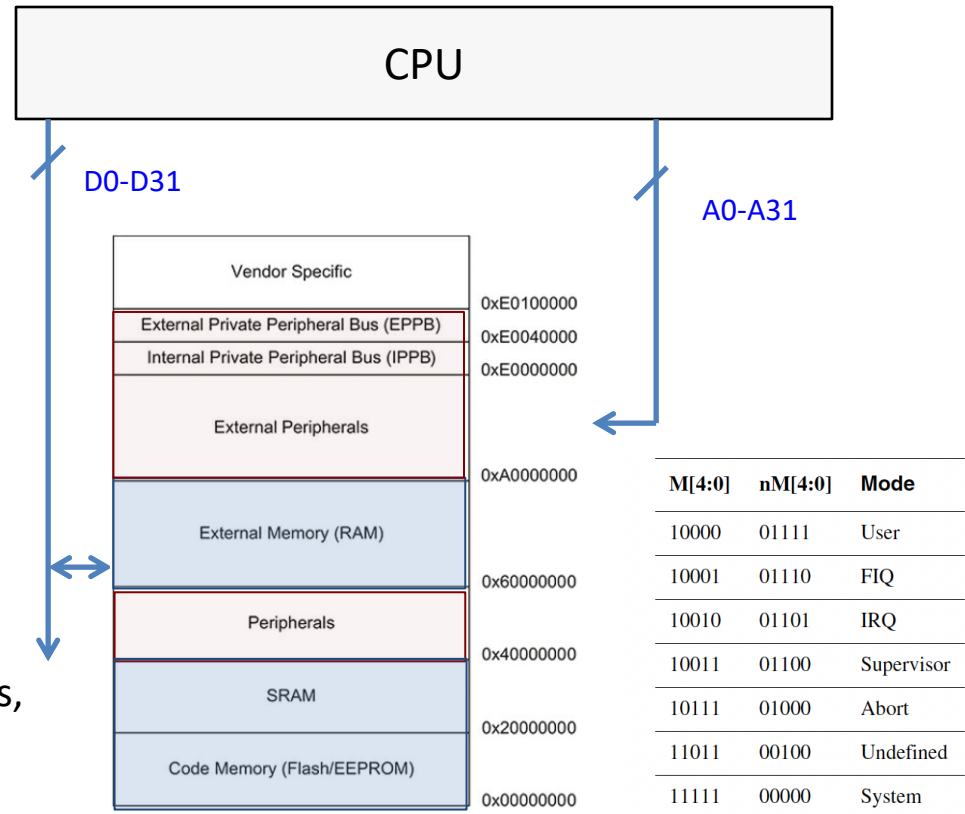- I/O ports are mapped on the memory address space
- Processor
 - Easy implementation
- Address decoding
 - **More complicated**
 - nWAIT is used for slow I/O devices
- OS viewpoint
 - Can't cause a trap when a user program accesses I/O ports.
 - Yet reserve I/O ports for OS accesses, using M[4:0]




Port-Mapped I/O

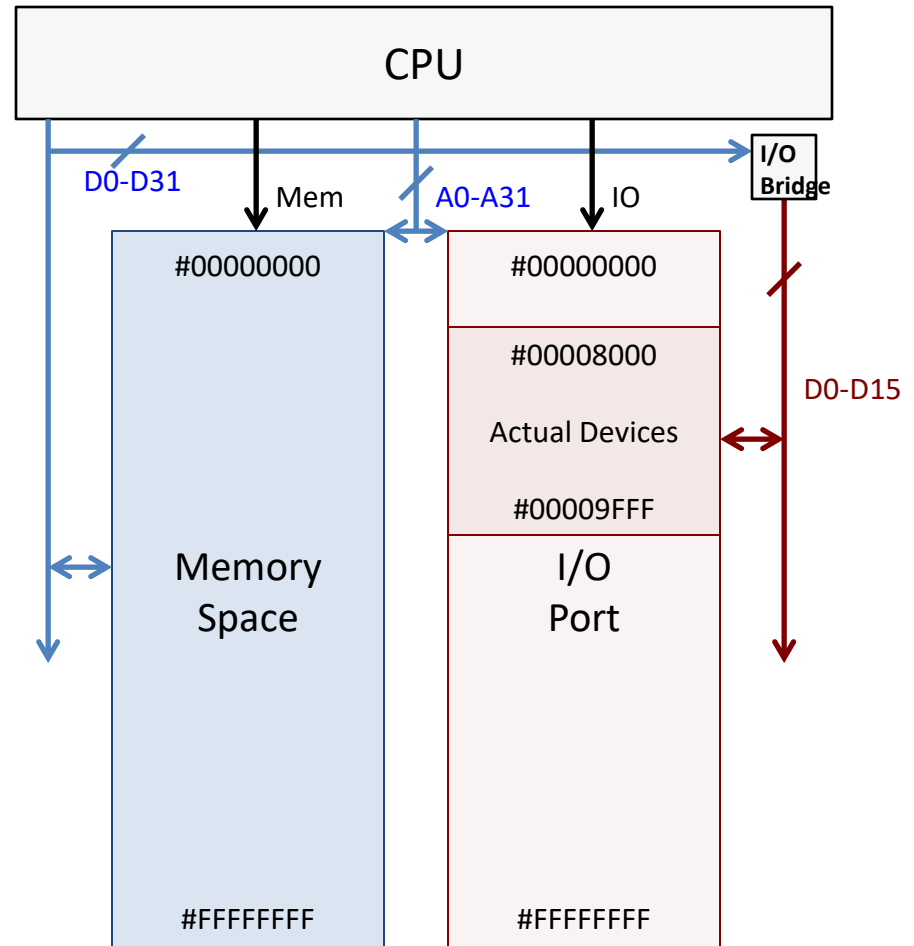- **I/O ports have a separate space** from the memory address space.
- **Processor**
 - Distinguishes data access and I/O operations
 - Needs a pin distinguish I/O and data memory access, such as IO/~M
- **Address decoding**
 - Easy
- **OS viewpoint**
 - Can cause a trap when a user program executes IN and OUT



Switching between Memory and I/O Address Spaces

 - IO/ \sim M distinguishes memory and I/O address spaces.
- \sim RD and \sim WR are shared among system memory and I/O devices



From Microprocessors and Microcontroller 1-15 8085 Microprocessor Architecture